

Design with Analog Multiplexers

Design with Analog Multiplexers

By

K.C. Selvam

**Cambridge
Scholars
Publishing**



Design with Analog Multiplexers

By K.C. Selvam

This book first published 2024

Cambridge Scholars Publishing

Lady Stephenson Library, Newcastle upon Tyne, NE6 2PA, UK

British Library Cataloguing in Publication Data

A catalogue record for this book is available from the British Library

Copyright © 2024 by K.C. Selvam

All rights for this book reserved. No part of this book may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording or otherwise, without the prior permission of the copyright owner.

ISBN: 978-1-0364-1519-8

ISBN (Ebook): 978-1-0364-1520-4

Dedicated to my loving wife
S. Latha (Late)

CONTENTS

Preface	x
Chapter 1	1
Introduction to Analog Multiplexers	
1.1 Transistor multiplexer	
1.2 FET multiplexer	
1.3 MOSFET multiplexer	
1.4 CD4053	
1.5 CD4052 and CD 4051	
1.6 555 Internal diagram	
Chapter 2	5
Waveform Generators	
2.1 Voltage to period converter	
2.2 Voltage to frequency converter	
2.3 Voltage controlled function generator - I	
2.4 Voltage controlled function generator - II	
Chapter 3	17
Analog Multipliers using Multiplexers	
3.1 Saw tooth wave referenced TDM	
3.2 Triangular wave referenced TDM	
3.3 TDM using no reference – type I	
3.4 TDM using no reference – type II	
3.5 TDM using 555 astable multivibrator	
3.5.1 Type I	
3.5.2 Type II	
3.6 TDM using 555 monostable multivibrator	
Chapter 4	41
Analog Dividers	
4.1 Saw tooth wave referenced TDD	
4.2 Triangular wave referenced TDD	
4.3 TDD using no reference – type I	
4.4 TDD using no reference – type II	

4.5 TDD using 555 astable multivibrator	
4.5.1 Type I	
4.5.2 Type II	
4.6 TDD using 555 monostable multivibrator	
4.6.1 Type I	
4.6.2 Type II	
Chapter 5	65
Multiplier-cum-Dividers	
5.1 Saw tooth wave referenced MCD	
5.1.1 Type I	
5.1.2 Type II	
5.1.3 Type III	
5.2 Triangular wave referenced MCD	
5.2.1 Type I	
5.2.2 Type II	
5.2.3 Type III	
5.3 MCD using 555 Astable multivibrator	
5.3.1 Type I	
5.3.2 Type II	
5.4 MCD using 555 monostable multivibrator	
Chapter 6	93
Analog Square Rooters	
6.1 Saw tooth wave referenced square rooter	
6.2 Triangular wave referenced square rooter	
6.3 Square rooter using no reference – type I	
6.4 Square rooter using no reference – type II	
6.5 Square rooter using 555 astable multivibrator	
6.5.1 Type I	
6.5.2 Type II	
6.6 Square rooter using 555 monostable multivibrator	
6.6.1 Type I	
6.6.2 Type II	
Chapter 7	117
Square Root of Multiplication	
7.1 Sawtooth wave referenced SRM	
7.2 Triangular wave referenced SRM	
7.3 Time division SRM with no reference – type I	
7.4 Time division SRM with no reference – type II	

7.5 Double dual slope peak responding SRM using FBC	
7.6 Double dual slope peak responding SRM using FF	
7.7 Pulse position peak responding SRMs	
7.8 Peak responding SRM using voltage tunable astable	
7.9 SRM using 555 astable	
7.10 SRM using 555 monostable	
Chapter 8	145
Vector Magnitude Circuits	
8.1 Sawtooth wave referenced VMC	
8.2 Triangular wave referenced VMC	
8.3 Time division VMC with no reference type I	
8.4 Time division VMC with no reference type II	
8.5 Double dual slope peak responding VMC using FBC	
8.6 Double dual slope peak responding VMC using FF	
8.7 Pulse position peak responding VMCs	
8.8 Peak responding VMC using voltage tunable astable	
Chapter 9	174
Logic Gates and Combinational Circuits	
9.1 NOT gate	
9.2 AND gate	
9.3 OR gate	
9.4 NAND gate	
9.5 NOR gate	
9.6 Ex-OR gate	
9.7 Ex-NOR gate	
9.8 Half adder	
9.9 Half subtractor	
9.10 Digital comparator	
9.11 Even parity generator	
9.12 Odd parity generator	
Chapter 10	206
Flip Flops using Analog Multiplexers	
10.1 SR flip flop	
10.2 Clocked RS flip flop	
10.3 D flip flop	
10.4 JK flip flop	
10.5 T flip flop	

PREFACE

The most popular analog multiplexer ICs CD4051, CD4052 and CD4053 are used for many electronic circuits. This book explains how they are used for (i) analog function circuits and (ii) digital circuits.

I am highly indebted to my

- (i) Mentor Prof. Dr. V.G.K. Murti who taught me about Function Circuits
- (ii) Philosopher Prof. Dr. P. Sankaran who taught me measurements and instrumentation
- (iii) Teacher Prof. Dr. K. Radha Krishna Rao who taught me operational amplifiers
- (iv) Gurunather Prof. Dr. V. Jagadeesh Kumar who guided me in the proper way of scientific world
- (v) Trainer Dr. M. Kumaravel who trained me to do experiments with analog multiplexers
- (vi) Promoter Prof. Dr. Bhaskar Ramamurthi who promoted me to higher post in IIT Madras
- (vii) Director Prof. Dr. V. Kamakoti who motivated me to do this work
- (viii) Encourager Prof. Dr. Enakshi Bhattacharya who encouraged me to get this result
- (ix) Leader Prof. Dr. Devendra Jalihal who kept me in a happy and peaceful official atmosphere
- (x) Supervisor Prof. Dr. Nagendra Krishnapura who monitored all my research work at IIT Madras

I also thank my friends Prof. Dr. R. Sarathi, Dr. Balaji Srinivasan, Dr. T.G. Venkatesh, Dr. Bharath Bhikkaji, Dr. Bobey George, Dr. S. Anirudhan, Dr. Aravind and Mrs. T. Padmavathy for their constant encouragement throughout my research work. I thank all other staff, students, and faculty of Electrical Engineering Department, Indian Institute of Technology Madras, for their immense help during the experimental setups, manuscript preparation and proof readings.

CHAPTER 1

INTRODUCTION TO ANALOG MULTIPLEXER

An analog multiplexer (also known as a MUX or data selector) is a device used to select one of many input signals and connect that selected input to a single output/transmission line. A select line is used to control which input is connected to the output of the multiplexer. An analog multiplexer incorporates analog switches to select one signal from multiple analog inputs and forward it to a single output line. The analog multiplexer can also be used as a demultiplexer since analog switches can transfer a signal bidirectionally. The multiplexer offers the benefit of reducing the required number of transmission lines by switching various signals onto a single line.

1.1 TRANSISTOR MULTIPLEXERS

Figure 1.1 shows analog multiplexer using transistors. If the control input CON is HIGH ($+V_{CC}$), transistor Q_1 is ON, Q_2 is OFF and (V_1) will appear at V_N . If the control input CON is LOW ($-V_{CC}$), transistor Q_1 is OFF, Q_2 is ON and (V_2) will appear at V_N . The operation is illustrated in table I.

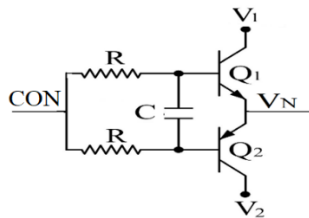


Fig. 1.1 Transistor multiplexer

Table I

CON	V_N
HIGH	V_1
LOW	V_2

1.2 JFET MULTIPLEXERS

Figure 1.2 shows analogue multiplexers using FETs. If the control input CON is HIGH ($+V_{CC}$), FETs Q_1 is ON, Q_2 is OFF and (V_1) will appear at V_N . If control input CON is LOW ($-V_{CC}$), FETs Q_1 is OFF, Q_2 is ON and (V_2) will appear at V_N . The operation is illustrated in Table II.

1.3 MOSFET MULTIPLEXER

Figure 1.3 shows analogue multiplexer using MOSFETs. If the control input CON is HIGH ($+V_{CC}$), MOSFETs Q_1 is ON, Q_2 is OFF and (V_1) will appear at V_N . If control input CON is LOW ($-V_{CC}$), MOSFETs Q_1 is OFF, Q_2 is ON and (V_2) will appear at V_N . The operation is illustrated in table III.

1.4 ANALOGUE MULTIPLEXER IC CD 4053

Fig. 1.4 shows the symbol of analogue triple 2 to 1 multiplexer. Each multiplexer has four terminals. In case of multiplexer M_1 , it has 'ay', 'ax', 'a' and 'A' terminals. In case of multiplexer M_2 , it has 'by', 'bx', 'b' and 'B' terminals. In case of multiplexer M_3 , it has 'cy', 'cx', 'c' and 'C' terminals.

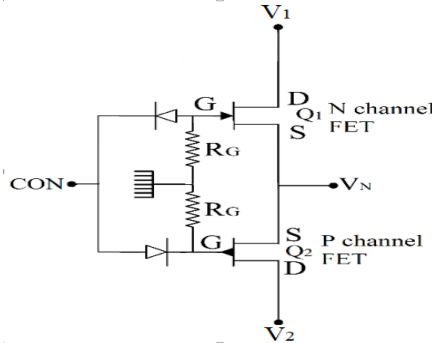


Fig.1.2 FET multiplexer

Table II

CON	V_N
HIGH	V_1
LOW	V_2

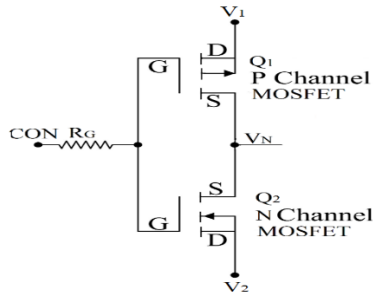


Fig. 1.3 MOSFET multiplexer

Table III

CON	V_N
HIGH	V_1
LOW	V_2

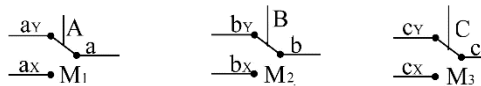


Fig. 1.4 Triple 2 to 1 multiplexers

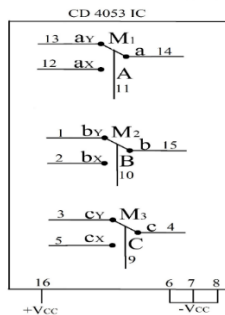


Fig. 1.5 Pin details of CD 4053 IC

In multiplexer M_1 , if the pin 'A' is HIGH, then 'ay' is connected to 'a' and if the pin 'A' is LOW, then 'ax' is connected to 'a'. In multiplexer M_2 , if the pin 'B' is HIGH, then 'by' is connected to 'b' and if the pin 'B' is LOW, then 'bx' is connected to 'b'. In multiplexer M_3 , if the pin 'C' is HIGH, then 'cy' is connected to 'c' and if the pin 'C' is LOW, then 'cx' is connected to 'c'.

All the three multiplexers M_1, M_2 and M_3 are available in one IC PACKAGE of CMOS CD4053 IC. The pin details of this CD4053 IC are given in the Fig. 1.5.

1.5 ANALOG MULTIPLEXERS CD4051 and CD4052

Fig. 1.6 shows pin details of analog multiplexer IC 4052. Fig. 1.7 shows pin details of analog multiplexer IC 4051.

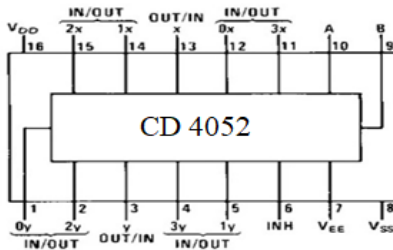


Fig. 1.6 pin details of IC 4052

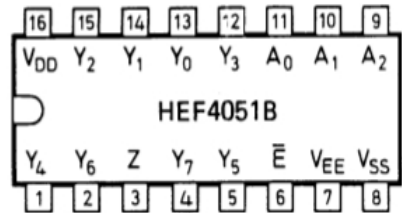


Fig. 1.7 pin details of IC 4051

1.6 INTERNAL DIAGRAM OF 555 TIMER

Fig. 1.8 shows the internal diagram of 555 timer.

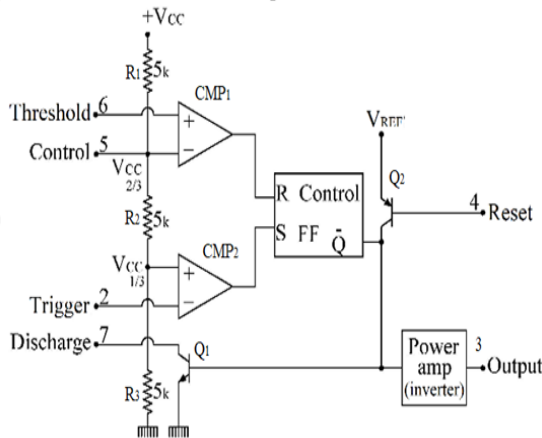


Fig. 1.8 Internal diagram of 555 timer

CHAPTER 2

WAVEFORM GENERATORS

The circuits which generate sine, square, pulse, saw tooth and triangular waveforms are discussed in this chapter. These waveforms are used in timing and control, signal carriers for information transmission and storage, sweep signals for information display, test signals for automatic test and measurement and audio signals for electronic music. The function of function generator is to produce a waveform of a particular frequency, amplitude, and shape and duty cycle. Sine wave oscillators are used to test the characteristics of low pass, high pass and band pass filters. Pulse waveforms are used to test digital circuits. Saw tooth and triangular waves are required to develop function circuits either internally or externally.

2.1 ASTABLE MULTIVIBRATOR

Fig. 2.1 shows an astable multivibrator using op-amp. Let us assume initially that the op-amp output is LOW (i.e., negative saturation). The voltage at the non-inverting terminal will be

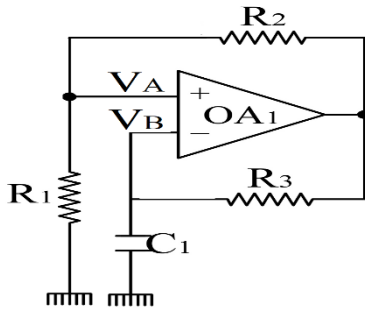


Fig. 2.4 astable multivibrator

$$V_A = \beta(-V_{SAT})$$

$$\beta = \frac{R_1}{R_1 + R_2} \quad (2.1)$$

The voltage at inverting terminal V_B will be positive w.r.t V_A and its potential is decreasing i.e., C_1 charges down through R_3 . When the potential difference between the two input terminals approaches zero, the op-amp comes out of saturation. The positive feedback from the output to terminal V_A causes regenerative switching which drives the op-amp to positive saturation. Capacitor C_1 charges up through R_3 and V_B potential rises exponentially; when it reaches $V_B = \beta(+V_{cc})$ the circuit switches back to the state in which op-amp is in negative saturation. The sequence therefore repeats to produce square waveform of time period T at its output. The time period T is given as

$$T = 2R_3C_1 \ln\left(1 + 2\frac{R_1}{R_2}\right) \quad (2.2)$$

Voltage to period converter: If in the astable multivibrator shown in Fig.2.1, the R_2 terminal is removed from the output terminal and an analog multiplexer is added between R_2 and output as shown in Fig. 2.2, then the circuit will work as voltage to time period converter. The time period T is given as

$$T = V_I K_1 \quad (2.3)$$

Where K_1 is a constant depends on equation (2.2) and op-amp saturation voltage or supply voltage V_{cc} .

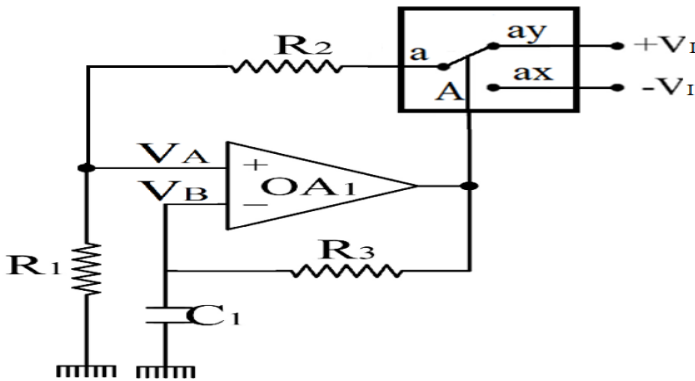


Fig. 2.2 voltage to period converter

Voltage to frequency converter: If in the astable multivibrator shown in Fig. 2.1, the R_3 terminal is removed from the output terminal and an analog multiplexer is added between R_3 and output as shown in Fig. 2.3, then the circuit will work as voltage to frequency converter. The frequency 'f' is given as

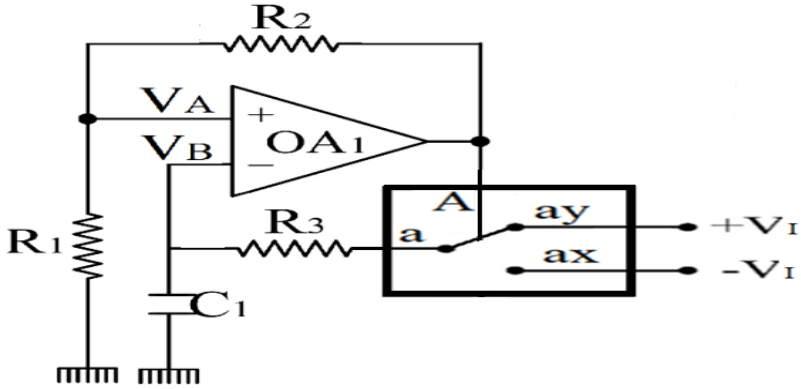


Fig. 2.3 voltage to frequency converter

$$f = V_I K_1 \quad (2.4)$$

Where K_1 is a constant depends on equation (2.6) and op-amp saturation voltage or supply voltage V_{CC} .

2.2 SAW TOOTH WAVE GENERATORS

Two circuits for generation of saw tooth wave are shown in Figs. 2.4 and their associated waveforms in Fig. 2.5. A saw tooth wave V_{S1} of peak value V_R and time period T is generated by these circuits.

In Fig. 2.4(a)

$$V_R = 2V_{BE} \quad (2.5)$$

$$T = 1.4R_1C_1 \quad (2.6)$$

In Fig. 2.4(b), if initially op amp OA_2 output is LOW, the multiplexer M_1 connects 'ax' to 'a' and the integrator formed by resistor R_1 , capacitor C_1 and op amp OA_1 integrates $(-V_R)$ and its output is given as

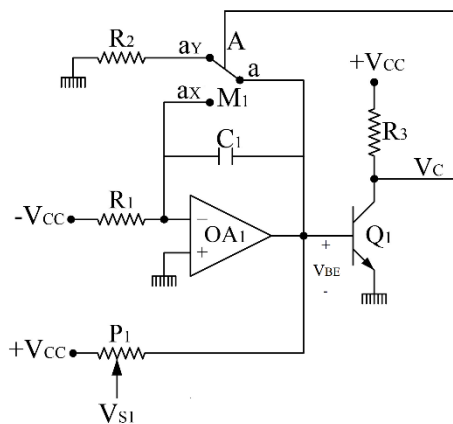


Fig. 2.4(a) Saw tooth wave generator – I

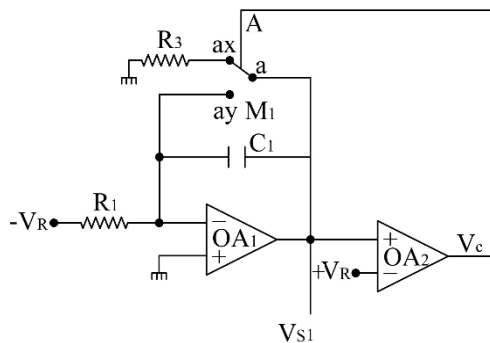


Fig. 2.4(b) Saw tooth wave generator – II

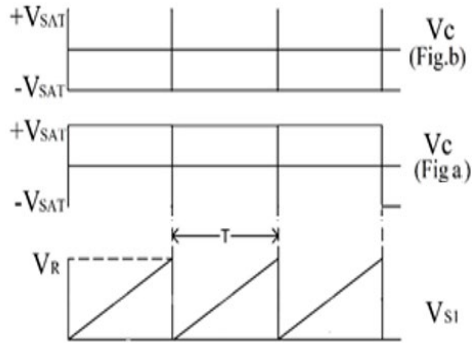


Fig. 2.5 associated waveforms of Fig. 2.4

$$V_{S1} = -\frac{1}{R_1 C_1} \int -V_R dt$$

$$V_{S1} = \frac{V_R}{R_1 C_1} t \quad (2.7)$$

A positive going ramp is generated at the output of op amp OA_1 and when it reaches the value of reference voltage $+V_R$ the comparator OA_2 output becomes HIGH. The multiplexer M_1 now connects 'ay' to 'a' and shorts capacitor C_1 and hence the integrator output becomes zero. Then the comparator output is LOW and the sequence therefore repeats to give a perfect saw tooth wave V_{S1} of peak value V_R at the output of op – amp OA_1 . From equation (2.7), Fig. 2.5 and fact that at $t = T$, $V_{S1} = V_R$.

$$V_R = \frac{V_R}{R_1 C_1} T$$

2.3 FUNCTION GENERATOR – TYPE I

A triangular wave V_{T1} with $\pm V_T$ peak to peak value and time period T is generated by the triangular wave generator shown in Figs. 2.6 and its associated waveforms are shown in Figs. 2.7.

The output of op amp OA_1 is a triangular wave V_{T1} with $\pm V_T$ peak values and time period of T . Initially the comparator OA_2 output is LOW ($-V_{SAT}$), the output of the integrator composed by op-amp OA_1 , resistor R_1 and capacitor C_1 , is given as

$$V_{T1} = -\frac{1}{R_1 C_1} \int -V_{SAT} dt = \frac{V_{SAT}}{R_1 C_1} t \quad (2.9)$$

The integrator output is rising towards positive saturation and when it reaches a value $+V_T$, the comparator output becomes HIGH($+V_{SAT}$). The output of the integrator composed by op-amp OA₁, resistor R₁ and capacitor C₁, is given as

$$V_{T1} = -\frac{1}{R_1 C_1} \int +V_{SAT} dt = -\frac{V_{SAT}}{R_1 C_1} t$$

Now the output of the integrator is changing its slope from $+V_T$ towards ($-V_T$) and when it reaches a value ' $-V_T$ ', the comparator output becomes LOW($-V_{SAT}$) and the sequence therefore repeats to give (i) a triangular waveform V_{T1} with $\pm V_T$ peak to peak values at the output of op-amp OA₁ and (ii) a square waveform V_C with $\pm V_{SAT}$ peak to peak values at the output of comparator OA₂.

From the waveforms shown in Fig. 2.7, from equation (2.9) and the fact that at $t = T/2$, $V_{T1} = 2V_T$

$$\begin{aligned} 2V_T &= \frac{V_{SAT}}{R_1 C_1} \frac{T}{2} \\ T &= \frac{4V_T R_1 C_1}{V_{SAT}} \end{aligned} \quad (2.10)$$

When the comparator OA₂ output is LOW ($-V_{SAT}$), the effective voltage at the non-inverting terminal of comparator OA₂ will be, by superposition principle,

$$\frac{(-V_{SAT})}{(R_2 + R_3)} R_2 + \frac{(+V_T)}{(R_2 + R_3)} R_3$$

When this effective voltage at the non-inverting terminal of comparator OA₂ becomes zero

$$\frac{(-V_{SAT})R_2 + (+V_T)R_3}{(R_2 + R_3)} = 0$$

$$(+V_T) = (+V_{SAT}) \frac{R_2}{R_3}$$

When the comparator OA₂ output is HIGH (+V_{SAT}), the effective voltage at the non-inverting terminal of comparator OA₂ will be by superposition principle

$$\frac{(+V_{SAT})}{(R_2 + R_3)} R_2 + \frac{(-V_T)}{(R_2 + R_3)} R_3$$

When this effective voltage at non-inverting terminal of comparator OA₂ becomes zero

$$\frac{(+V_{SAT})R_2 + (-V_T)R_3}{(R_2 + R_3)} = 0$$

$$(-V_T) = (-V_{SAT}) \frac{R_2}{R_3}$$

$$\pm V_T = \pm V_{SAT} \frac{R_2}{R_3} \approx 0.76(\pm V_{CC}) \frac{R_2}{R_3} \quad (2.11)$$

From equation (2.10) and (2.11), time period T of the generated triangular/square waveforms is given as

$$T = 4R_1C_1 \frac{R_2}{R_3} \quad (2.12)$$

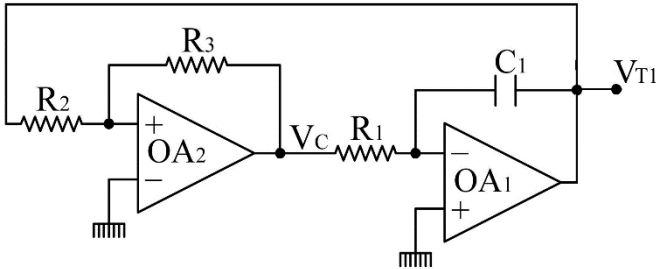


Fig. 2.6 triangular wave generator

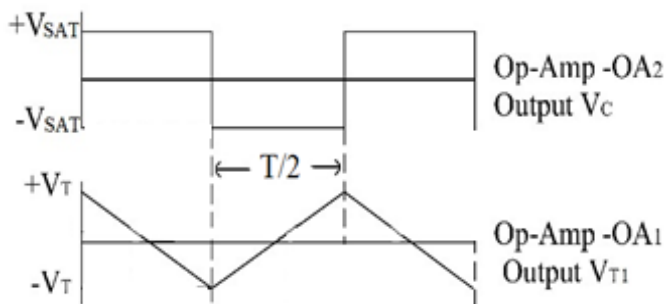


Fig. 2.7 associated waveforms of Fig. 2.6

The triangular wave generator shown in Fig. 2.6 can be converted to a voltage-controlled function generator by adding an analog multiplexer between comparator and integrator as shown in Fig. 2.8.

$$T = \frac{4V_T R_1 C_1}{V_I} \quad (2.23)$$

$$T = \frac{4R_1 C_1}{V_I} \frac{R_2}{R_3} \quad (2.24)$$

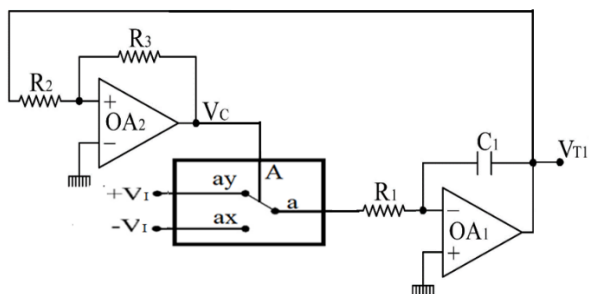


Fig. 2.8 function generator

2.4 FUNCTION GENERATOR – TYPE II

The circuit diagram of the function generator – type II is shown in Fig. 2.9 and its associated waveforms are shown in Fig. 2.10.

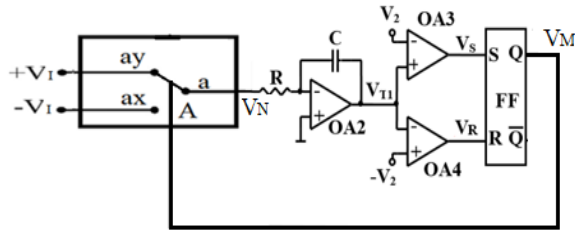


Fig. 2.9 Function generator – type II

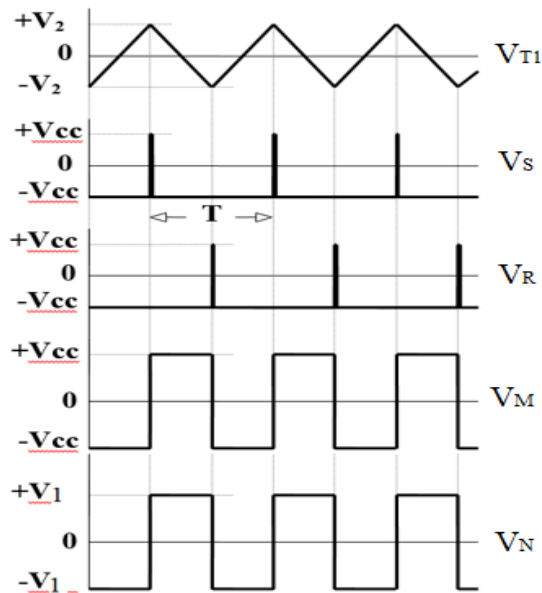


Fig. 2.10 Associated Waveforms of Fig. 2.9

Let initially the SR flip flop output Q be LOW. The multiplexer selects $-V_1$ ('ax' is connected to 'a'). $-V_1$ will be given to the integrator formed by OA₂, resistor R and capacitor C. Its output will be

$$V_{T1} = -\frac{1}{RC} \int -V_1 dt = \frac{V_1}{RC} t \quad (2.25)$$

The output of integrator OA2 is a positive going ramp. When the output of the integrator exceeds the other input voltage V_2 , SR Flip flop output Q is

set to HIGH by the comparator OA₃. The multiplexer selects +V₁ ('ay' is connected to 'a') and +V₁ is given to the integrator OA₂. Now the integrator output will be

$$V_{T1} = -\frac{1}{RC} \int V_1 dt = -\frac{V_1}{RC} t \quad (2.26)$$

The output of the integrator is changing its slope from positive to negative. When the output of the integrator exceeds the input voltage $-V_2$, SR flip flop output 'Q' will be reset to LOW by the comparator OA₄ and the cycle therefore repeats. From the equation (2.26) and from the waveforms shown in Fig. 2.10 at $t = T/2$, $V_T(t) = 2V_2$

$$2V_2 = \frac{V_1}{2RC} T \quad (2.27)$$

$$T = \frac{V_2}{V_1} 4RC, \quad f = \frac{V_1}{V_2} \frac{1}{4RC} \quad (2.28)$$

WORKED EXAMPLES:

2.1 Design a square wave generator for frequency of 1KHz. Power supply voltage of $\pm 15V$.

The square wave generator or astable multivibrator is given in Fig. 2.1. From equation (2.2)

$$T = 2R_3 C_1 \ln\left(1 + 2 \frac{R_1}{R_2}\right)$$

Given; frequency = 1kHz

$$T = 1/f = 1\text{mS}$$

$$\text{Let } R_2 = 1.16R_1$$

$$\text{Let } R_1 = 10K, \text{ then } R_2 = 11.6K$$

$$T = 2R_3 C_1 \ln 2.7241 = 2R_3 C_1$$

$$R_3 = \frac{T}{2C_1}$$

$$\text{Let } C_1 = 0.05\mu F,$$

$$R_3 = \frac{1 \times 10^{-3}}{2 \times 0.05 \times 10^{-6}} = 10K$$

2.2 Design a saw tooth wave generator with peak value of 5V and time period of 1mS.

The saw tooth wave generator is shown in Fig. 2.5. Chose $V_R = 5V$ with LM3365V reference diode. Given: $T = 1mS$. Let $R_1 = 1M$.

From equation (2.8)

$$T = R_1 C_1, \quad C_1 = \frac{T}{R_1} = \frac{1 \times 10^{-3}}{1 \times 10^6} = 1nF$$

2.3 Design a triangular wave generator of time period 20mS with 10V peak volts. Power supply is $\pm 15V$.

The triangular wave generator circuit is shown in Fig. 2.6. Given: $T = 20mS$, $V_T = 10V$, $V_{CC} = 15V$

From equation (2.11)

$$\pm V_T = \pm V_{SAT} \frac{R_2}{R_3} \square 0.76(\pm V_{CC}) \frac{R_2}{R_3}$$

Let $R_2 = 10K$

$$R_3 = \frac{R_2 0.76 V_{CC}}{V_T} = 11.4K$$

From equation (2.12)

$$T = 4R_1 C_1 \frac{R_2}{R_3} = 3.5 R_1 C_1$$

Let $C_1 = 0.1\mu F$

$$R_1 = \frac{T}{3.5 C_1} = \frac{20 \times 10^{-3}}{3.5 \times 0.1 \times 10^{-6}} = 57.14K$$

2.4 Design a voltage controlled triangular wave generator of 1KHz frequency and 10V peak value. The given control voltage is (-1V). Power supply used is $\pm 15V$.

Given: $f = 1\text{KHz}$; $T = 1/f = 1\text{ms}$, $V_1 = -1\text{V}$, $V_T = 10\text{V}$, $V_{CC} = 15\text{V}$

The voltage controlled triangular wave generator is shown in Fig. 2.8

$$\pm V_T = \pm V_{SAT} \frac{R_3}{R_4} \square 0.76(\pm V_{CC}) \frac{R_3}{R_4}$$

$$R_4 = 0.76(V_{CC}) \frac{R_3}{V_T}$$

Let $R_3 = 10\text{K}$

$$R_4 = 0.76 \times 15 \times \frac{10 \times 10^3}{10} = 11.4 \text{ K}$$

From equation (2.28)

$$f = \frac{-V_I}{4RCV_T}$$

Let $C = 0.1\mu\text{F}$

$$R = \frac{-V_I}{4fCV_T} = \frac{1}{4 \times 1 \times 10^3 \times 0.1 \times 10^{-6} \times 10} = 250\Omega$$

CHAPTER 3

ANALOG MULTIPLIERS USING MULTIPLEXERS

If the width of a pulse train is made proportional to one voltage and the amplitude of the same pulse train to a second voltage, then the average value of this pulse train is proportional to the product of two voltages, and is called time division multiplier or pulse averaging multiplier or sigma delta multiplier. The time division multiplier can be implemented using (1) triangular wave (2) saw tooth wave and (3) without using any reference wave.

Peak responding multipliers are classified in to (i) peak detecting multipliers and (ii) peak sampling multipliers. A short pulse/saw tooth waveform whose time period ' T ' is proportional to one voltage is generated. Another input voltage is integrated during the time period ' T '. The peak value of the integrated voltage is proportional to the product of the two input voltages. This is called double single slope peak responding multiplier. A square/triangular waveform whose time period ' T ' is proportional to one voltage is generated. Another input voltage is integrated during the time period ' T '. The peak value of the integrated voltage is proportional to the product of the two input voltages. This is called double dual slope peak responding multiplier. A rectangular pulse waveform whose OFF time is proportional to one voltage is generated. Another voltage is integrated during this OFF time. The peak value of integrated output is proportional to the product of the two input voltages. This is called pulse width integrated peak responding multiplier. At the output stage of a peak responding multiplier, if peak detector is used, it is called peak detecting multiplier and if sample & hold is used, it is called peak sampling multiplier. The principles of peak responding multipliers are described in this chapter.

3.1 SAW TOOTH WAVE REFERENCED TIME DIVISION MULTIPLIER

The time division multiplier using saw tooth wave as reference is shown in Fig. 3.1 and its associated waveforms in Fig.3.2. A saw tooth wave V_{S1} of peak value V_R is compared with one input voltage V_1 by the op-amp OA

and a rectangular wave V_M is produced at the output of op-amp OA. The ON time ' δ_T ' of the rectangular wave V_M , is given as

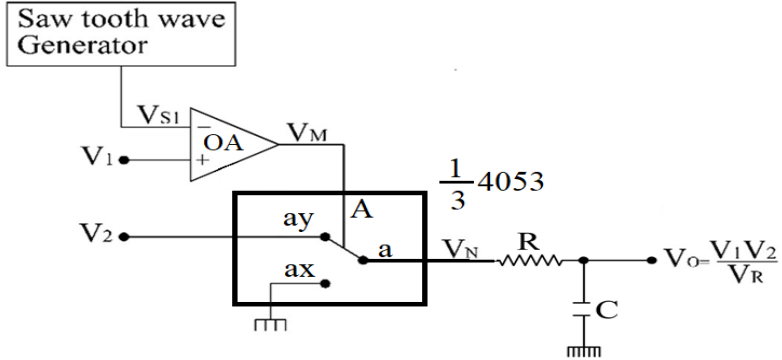


Fig. 3.1 Saw tooth wave referenced time division multiplier

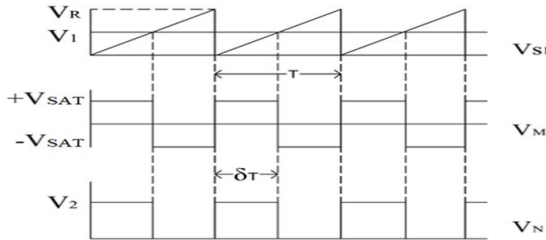


Fig.3.2 Associated Waveforms of Fig.3.1

$$\delta_T = \frac{V_1}{V_R} T \quad (3.1)$$

This rectangular wave V_M controls the analog multiplexer A. The analog multiplexer A is connecting (i) another input voltage V_2 during the ON time " δ_T " of rectangular pulse V_M ('ay' is connected to 'a') and (ii) zero volts during OFF time of rectangular pulse V_M ('ax' is connected to 'a'), to the resistor (R) - capacitor (C) low pass filter (LPF). Another rectangular pulse waveform V_N is generated at the output of analog multiplexer A with V_2 as peak value and time period of same ' T '. The resistor (R) - capacitor (C) low pass filter (LPF) at the output stage gives average value ' V_O ' of the pulse train ' V_N '

$$V_O = \frac{1}{T} \int_0^{\delta_T} V_2 dt$$

$$V_O = \frac{1}{T} V_2 \delta_T$$

$$V_O = \frac{V_1 V_2}{V_R} \quad (3.2)$$

3.2 TRIANGULAR WAVE REFERENCED TIME DIVISION MULTIPLIER

The time division multiplier using a triangular wave as a reference clock is shown in Fig 3.3 and its associated waveforms in Fig. 3.4.

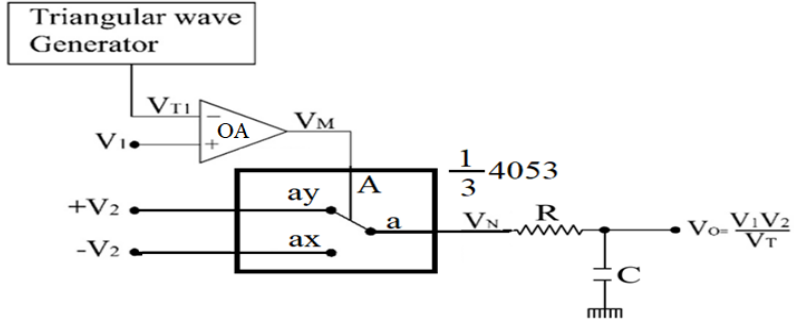


Fig. 3.3 Triangular wave referenced time division multiplier

A triangular wave V_{T1} of $\pm V_T$ peak to peak value is compared with the input voltage V_1 by the op-amp OA and a asymmetrical wave V_M is generated. The OFF time ' T_1 ' of this rectangular wave V_M is given as

$$T_1 = \frac{V_T - V_1}{2V_T} T \quad (3.3)$$

The ON time ' T_2 ' of this rectangular wave V_M is given as

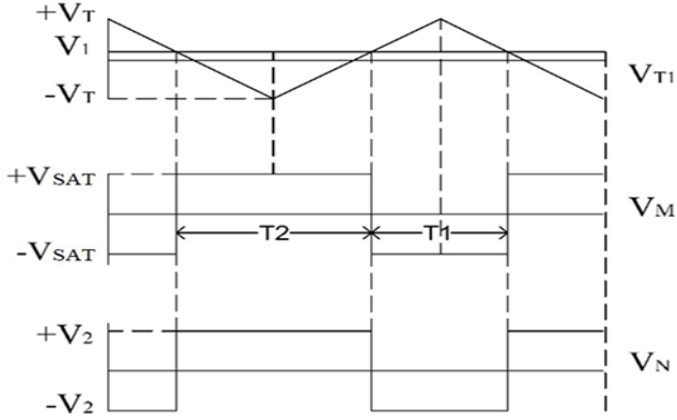


Fig. 3.4 Associated waveforms of Fig. 3.3

$$T_2 = \frac{V_T + V_1}{2V_T} T \quad (3.4)$$

The rectangular pulse V_M controls analog multiplexer A. The analog multiplexer A connects the other input voltage ($+V_2$) during ON time T_2 ('ay' is connected to 'a') and ($-V_2$) during OFF time T_1 of the rectangular pulse V_M ('ax' is connected to 'a') to the resistor (R) - capacitor (C) low pass filter (LPF). Another rectangular wave V_N with $\pm V_2$ maximum values is generated at the output of analog multiplexer A. The resistor (R) - capacitor (C) low pass filter (LPF) gives average value (V_O) of this pulse train V_N and is given as

$$V_O = \frac{1}{T} \left[\int_0^{T_2} (+V_2) dt + \int_{T_2}^{T_1+T_2} (-V_2) dt \right]$$

$$V_O = \frac{1}{T} (T_2 - T_1) V_2 \quad (3.5)$$

Equations (3.3) and (3.4) in (3.5) gives